

Last Name: _____ First Name _____ Network-ID _____

Discussion Section: _____ Discussion TA Name: _____

Turn off your cell phone and put it out of sight.

Keep your calculator on your own desk. Calculators cannot be shared.

This is a closed book exam. You have ninety (90) minutes to complete it.

1. Use a #2 pencil. Do not use a mechanical pencil or pen. Darken each circle completely, but stay within the boundary. If you decide to change an answer, erase vigorously; the scanner sometimes registers incompletely erased marks as intended answers; this can adversely affect your grade. Light marks or marks extending outside the circle may be read improperly by the scanner. Be especially careful that your mark covers the **center** of its circle.

2. You may find the version of **this Exam Booklet at the top of page 2**. Mark the version circle in the TEST FORM box near the middle of your answer sheet. **DO THIS NOW!**

3. Print your **NETWORK ID** in the designated spaces at the *right* side of the answer sheet, starting in the left most column, then **mark the corresponding circle** below each character. If there is a letter "o" in your NetID, be sure to mark the "o" circle and not the circle for the digit zero. If and only if there is a hyphen "-" in your NetID, mark the hyphen circle at the bottom of the column. When you have finished marking the circles corresponding to your NetID, check particularly that you have not marked two circles in any one of the columns.

4. Print **YOUR LAST NAME** in the designated spaces at the *left* side of the answer sheet, then mark the corresponding circle below each letter. Do the same for your **FIRST NAME INITIAL**.

5. Print your UIN# in the STUDENT NUMBER designated spaces and mark the corresponding circles. You need not write in or mark the circles in the SECTION box.

6. Sign your name (**DO NOT PRINT**) on the **STUDENT SIGNATURE line**.

7. On the **SECTION line**, print your **DISCUSSION SECTION**. You need not fill in the COURSE or INSTRUCTOR lines.

*Before starting work, check to make sure that your test booklet is complete. You should have 9 **numbered pages** plus three (3) Formula Sheets following these instructions.*

Academic Integrity—Giving assistance to or receiving assistance from another student or using unauthorized materials during a University Examination can be grounds for disciplinary action, up to and including dismissal from the University.

This Exam Booklet is Version A. Mark the **A** circle in the **TEST FORM** box near the middle of your answer sheet. **DO THIS NOW!**

Exam Grading Policy—

The exam is worth a total of **99** points, composed of three types of questions.

MC5: *multiple-choice-five-answer questions, each worth 6 points.*

Partial credit will be granted as follows.

- (a) If you mark only one answer and it is the correct answer, you earn **6** points.
- (b) If you mark *two* answers, one of which is the correct answer, you earn **3** points.
- (c) If you mark *three* answers, one of which is the correct answer, you earn **2** points.
- (d) If you mark no answers, or more than *three*, you earn **0** points.

MC3: *multiple-choice-three-answer questions, each worth 3 points.*

No partial credit.

- (a) If you mark only one answer and it is the correct answer, you earn **3** points.
- (b) If you mark a wrong answer or no answers, you earn **0** points.

MC2: *multiple-choice-two-answer questions, each worth 2 points.*

No partial credit.


- (a) If you mark only one answer and it is the correct answer, you earn **2** points.
- (b) If you mark the wrong answer or neither answer, you earn **0** points.

Some helpful information:

- A reminder about prefixes: p (pico) = 10^{-12} ; n (nano) = 10^{-9} ; μ (micro) = 10^{-6} ; m (milli) = 10^{-3} ; k (kilo) = 10^{+3} ; M or Meg (mega) = 10^{+6} ; G or Gig (giga) = 10^{+9} .

The next three questions pertain to the situation described below.

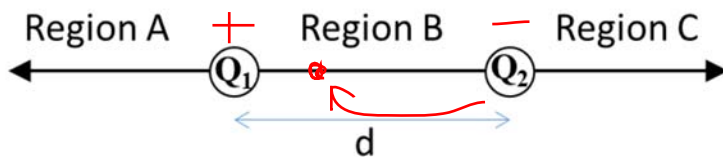A positive and a negative charge have mass 0.4 kg and are fixed in position along the x-axis separated by a distance $d=0.2$ m as shown in below.



$Q_1 = 8.2 \times 10^{-6}$ Coulombs
 $Q_2 = -1.64 \times 10^{-5}$ Coulombs
 $d = 0.2$ m
 $m = 0.4$ kg

1) If charge Q_2 is released from rest, how fast will it be moving when it is a distance $d/4$ from charge Q_1 ?

This is an energy conservation problem.

a. 11 m/s Initial potential energy: $U_0 = kQ_1Q_2/d$, initial kinetic energy: $K_0 = 0$.

b. 12.3 m/s Final potential: $U_1 = kQ_1Q_2/(d/4)$, $K_1 = mv^2/2$.

c. 5.5 m/s The conservation of energy implies

d. 9.53 m/s $kQ_1Q_2/d = mv^2/2 + 4kQ_1Q_2/d$

e. 0 m/s


$$\text{so } mv^2/2 = -3kQ_1Q_2/d \rightarrow v^2 = 2 \times 3(9 \times 10^9)(8.2 \times 10^{-6})(1.64 \times 10^{-5}) / (0.2 \times 0.4)$$

$$= 9077 \times 10^{9-11} = (9.527)^2$$

2) In which region(s) is there a point on the x-axis where the electric field due to the two charges is zero?

- a. Region A only
- b. Region A and B.
- c. Region B only.

possible 0 here.

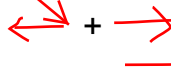

larger |charge|

3) In which region(s) is there a point on the x-axis where the electric potential due to the two charges is zero?


Potential is like a landscape: + makes a peak, and - a pit.

- a. Region B only.
- b. Region A only.
- c. Regions A and B.

In the present case the pit is 'much deeper', so the peak is inside the dip. Therefore there is a zero equipotential contour around the + charge.

The next three questions pertain to the situation described below.

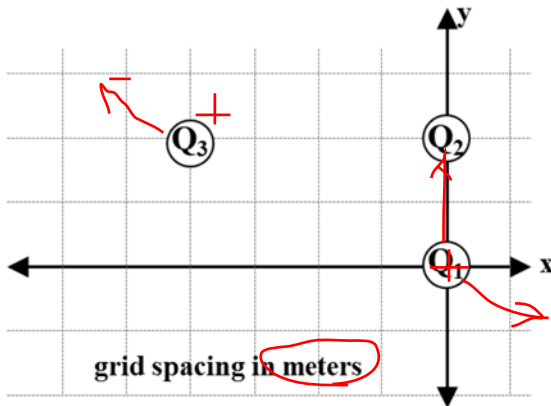Three charges are fixed in position as shown in below. Note, charges Q1 and Q3 are positive, charge Q2 is negative.



$$Q1 = 2.4 \times 10^{-6} \text{ Coulombs}$$

$$Q2 = -4.8 \times 10^{-6} \text{ Coulombs}$$

$$Q3 = 2.4 \times 10^{-6} \text{ Coulombs}$$

Recall superposition principle.
You can consider each charge separately.

I strongly recommend you to draw forces in the figure.

4) What is the x component of the force on charge Q1 due to the other two charges?

- a. $F_{1x} = -0.0236 \text{ N}$
- b. $F_{1x} = 0.00116 \text{ N}$
- c. $F_{1x} = 0.00232 \text{ N}$
- d. $F_{1x} = 0.00259 \text{ N}$
- e. $F_{1x} = -0.0259 \text{ N}$

This is only due to Q3.

$$\begin{aligned} \text{x comp of } F_{13} &= [kQ_3Q_1 / (2^2 + 4^2)] \times (4 / \sqrt{2^2 + 4^2}) \\ &= [(9 \times 10^9)(2.4 \times 10^{-6})(2.4 \times 10^{-6}) / 20] \times (2 / \sqrt{5}) \\ &= 2.318 \times 10^{-9-12} \text{ N} \end{aligned}$$

Here, Q1-Q3 in the formula are absolute values.

5) What is the y component of the force on charge Q1 due to the other two charges?

- a. $F_{1y} = 0.0233 \text{ N}$
- b. $F_{1y} = -0.0233 \text{ N}$
- c. $F_{1y} = 0.0224 \text{ N}$
- d. $F_{1y} = -0.0282 \text{ N}$
- e. $F_{1y} = 0.0248 \text{ N}$

Q3 and Q2 may be considered separately.

$$\begin{aligned} \text{y comp of } F_{13} &= -[kQ_3Q_1 / 20] \times (2 / \sqrt{20}) = -2.318 \times 10^{-3} \times (1/2) \\ \text{y comp of } F_{12} &= [kQ_2Q_1 / 2^2] = (9 \times 10^9)(4.8 \times 10^{-6})(2.4 \times 10^{-6}) / 4 \\ &= 25.9 \times 10^{9-12} = 25.9 \times 10^{-3} \end{aligned}$$

Adding these $F_{1y} = 24.75 \times 10^{-3} \text{ N}$

The sign is best determined by the figure.

that is, when the configuration is constructed

6) How much work does the electric field do, when the charges are brought from infinitely far away, to their location in the figure.

I recommend you to obtain the work YOU must do (and then flip the sign).

- a. $W_E = -0.0143 \text{ J}$
- b. $W_E = -0.0662 \text{ J}$
- c. $W_E = 0.0662 \text{ J}$
- d. $W_E = 0.0143 \text{ J}$
- e. $W_E = 0 \text{ J}$

The potential energy stored in the configuration is


$$\begin{aligned} &kQ_1Q_2/2 + kQ_2Q_3/4 + kQ_3Q_1/\sqrt{20} \\ &= (9 \times 10^9)(10^{-12})(-2.4 \times 4.8/2 - 4.8 \times 2.4/4 + 2.4 \times 2.4/\sqrt{20}) \\ &= 9 \times 10^{-3}(-5.76 - 2.88 + 1.31) = -66 \times 10^{-3} \text{ J} \end{aligned}$$

Thus, we must get 0.066 J by assembling the charges. That is, our work expenditure is -0.066 J. Therefore, the field does +0.066 J (by convention).

not a good question

The next two questions pertain to the situation described below.

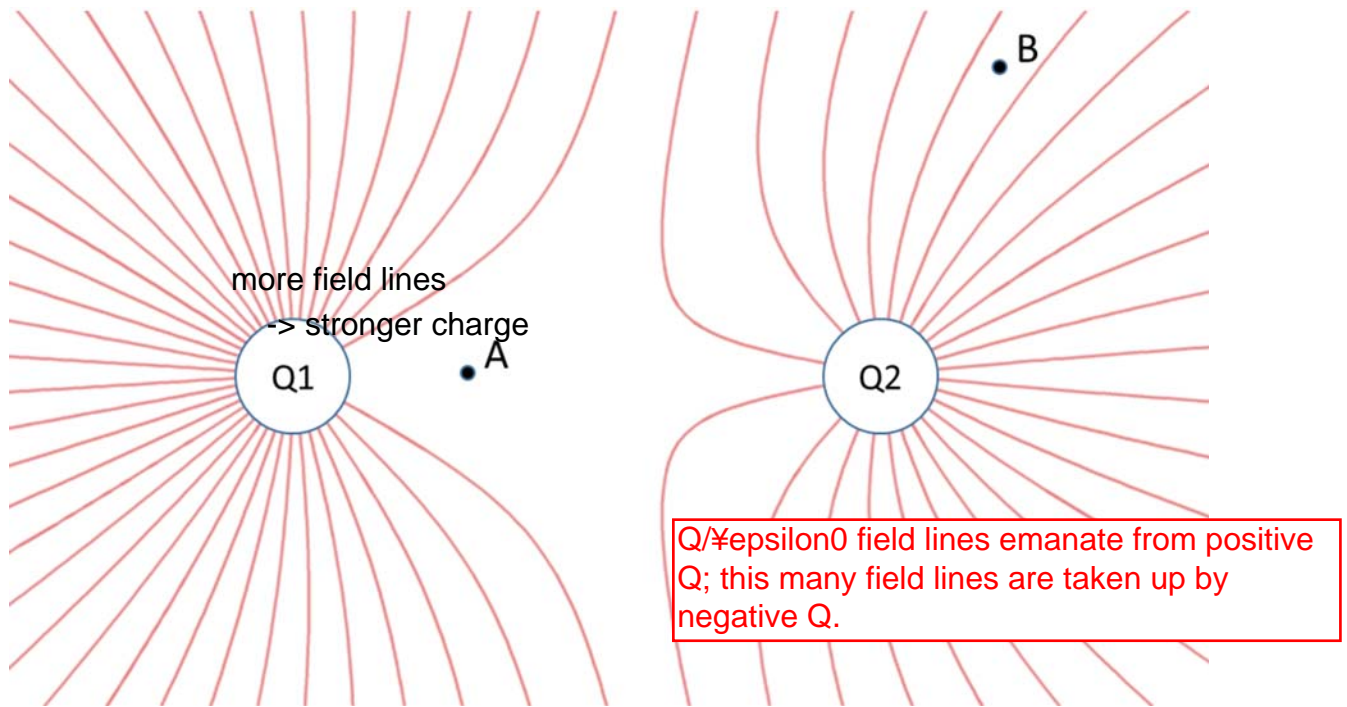The figure below shows the field lines due to two unknown point charges.



7) Compare the magnitude of the two charges.


- a. $|Q1| < |Q2|$
- b. $|Q1| > |Q2|$
- c. $|Q1| = |Q2|$

8) Compare the magnitude of the electric field at points A and B.

- a. $|E_A| > |E_B|$
- b. $|E_A| = |E_B|$
- c. $|E_A| < |E_B|$

The next three questions pertain to the situation described below.

Consider the circuit shown below.

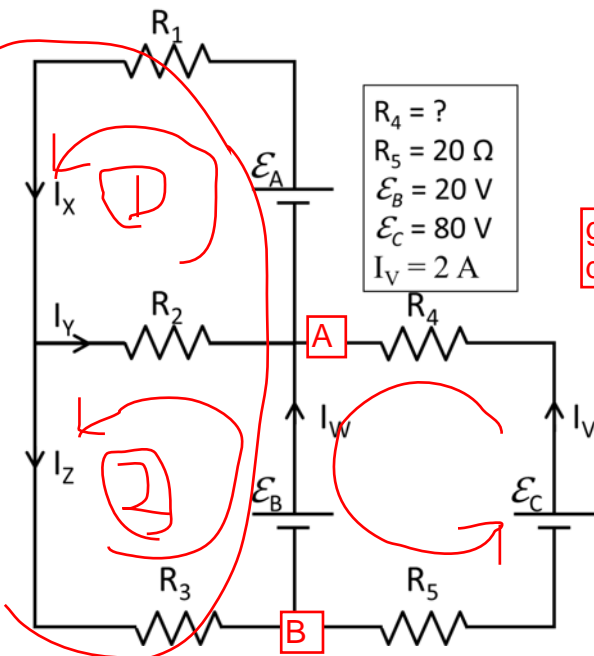

Kirchhoff's current law:
in current = out current
Kirchhoff's voltage law:
no voltage change around a loop

going down going down going up going down
← signs can be understood in this fashion.

The best method is to use the loop current approach. If we go around the loop we come back to the same potential.

Let us start from A along the loop:
 $-E_B - R_5 I_v + 80 - R_4 I_v = 0$
 or
 $-20 - 40 + 80 - 2R_4 = 0 \quad 20 = 2R_4 \rightarrow R_4 = 10 \text{ ohm.}$

Kirchhoff's voltage law

Another approach:
 $60 = (R_4 + R_5) I_v = 2R_4 + 40.$

This is ultimately due to the conservation of charge.

9) What is the resistance of resistor R_4 ?

- a. $R_4 = 5 \Omega$
- b. $R_4 = 10 \Omega$
- c. There is no value of R_4 for which $I_v = 2 \text{ A}$.
- d. $R_4 = 20 \Omega$
- e. $R_4 = 2 \Omega$

10) Which of the following equations is a valid application of Kirchhoff's current law?

- a. ~~$I_x + I_y = I_z$~~
 - b. ~~$I_z = I_w + I_v$~~
 - c. $I_y + I_w + I_v - I_x = 0$
- $I_x = I_y + I_z$ according to the figure.
 At A: in $I_y + I_v + I_w$ out $I_x \rightarrow I_x = I_y + I_v + I_w$
 At B: $I_z = I_v + I_w$


11) Which of the following equations is **NOT** a valid application of Kirchhoff's voltage law?

- a. $\epsilon_A + \epsilon_B - I_x R_1 - I_z R_3 = 0$
- b. $\epsilon_B - I_y R_2 - I_z R_3 = 0$
- c. $\epsilon_A - I_x R_1 - I_y R_2 = 0$

For loop 1 $\epsilon_A - R_1 I_x - R_2 I_y = 0$
 For loop 2 $\epsilon_B + R_2 I_y - R_3 I_z = 0$
 For loop 3 $\epsilon_B + \epsilon_A - R_1 I_x - R_3 I_z = 0$

The next four questions pertain to the situation described below.

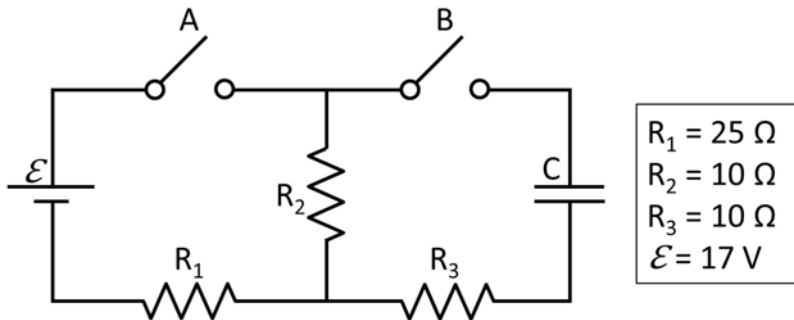Consider the circuit shown below. Initially, both switches are open and the capacitor has been charged to 10 Volts.




At time $t=0$ switch B is closed (switch A remains open).

12) What is the current through resistor R_3 just after the switch B is closed?


- a. $I_3 = 1.5 \text{ A}$. Initially C provides 10 V across $R_2 + R_3 = 20 \text{ ohms}$
- b. $I_3 = 0.5 \text{ A}$.
- c. $I_3 = 2.5 \text{ A}$.

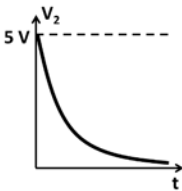13) Which of the following plots best represents the voltage V_2 across resistor 2 starting just after switch B is closed? (Be careful image is above answer choice)




Initially, 5 V across R_2 .
Eventually, zero V.

a.

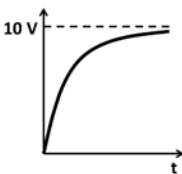


b.

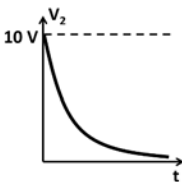

c.

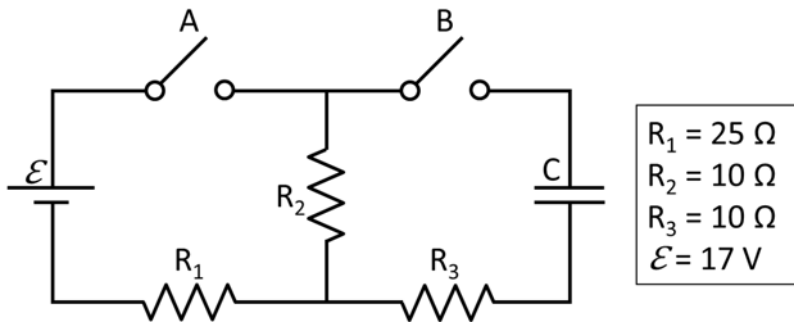14) Figure repeated from previous page

Consider the circuit shown below. Initially, both switches are open and the capacitor has been charged to 10 Volts. At time $t=0$ switch B is closed (switch A remains open).



If it takes $12 \mu\text{s}$ for the charge on the capacitor to drop the $1/2$ of its initial value, what is the capacitance of the capacitor C?

- a. $C = 1631 \text{ nF}$
- b. $C = 493 \text{ nF}$
- c. $C = 3370 \text{ nF}$
- d. $C = 866 \text{ nF}$
- e. $C = 215 \text{ nF}$

The half time is $\ln 2 RC = 0.693 RC$, where $R = 20$, so


$$12 \times 10^{-6} = 0.693 \times 20 \times C.$$

$$\text{Therefore, } C = 0.866 \times 10^{-6} \text{ F}$$

15) After a very long time, switch A is closed. Switch B remains closed. What is the magnitude of the current I_1 through resistor R_1 immediately after switch A is closed?

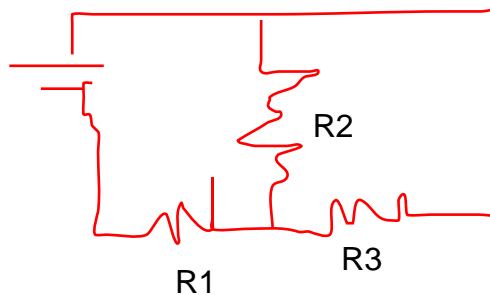
- a. $I_1 = 0.567 \text{ A}$
- b. $I_1 = 0.165 \text{ A}$
- c. $I_1 = 0.202 \text{ A}$
- d. $I_1 = 0.446 \text{ A}$
- e. $I_1 = 0.930 \text{ A}$

Immediately after $t = 0$, the voltage across $C = 0$, so the equivalent circuit looks as



$$\text{The total resistance} = 25 + 100/(10+10) = 30 \text{ } \Omega. \text{ Thus, } I = 17/30 = 0.567 \text{ A}$$

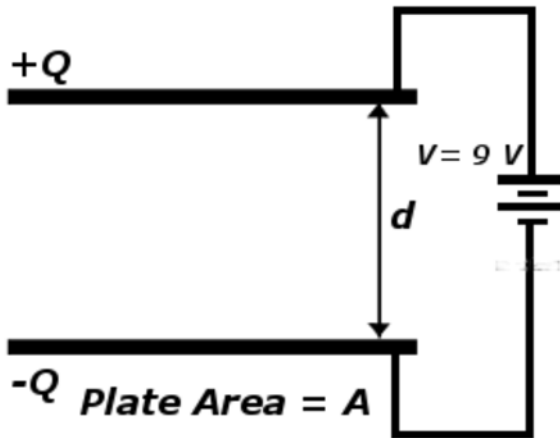The next three questions pertain to the situation described below.



This should not be read as m.m²,

A parallel plate capacitor consists of two metal plates with an area $A = 542 \text{ mm}^2$ separated by a distance $d = 0.36 \text{ mm}$. The capacitor is connected to a 9 volt battery as shown above.

16) What is the charge Q on the capacitor?

- a. $Q = 0.539 \text{ nC}$
- b. $Q = 1.08 \text{ nC}$
- c. $Q = 120 \text{ nC}$
- d. $Q = 0.12 \text{ nC}$
- e. $Q = 1.2 \times 10^{-4} \text{ nC}$

$$\begin{aligned}
 C &= \epsilon_0 A/d \\
 &= (8.85 \times 10^{-12}) (542 \times 10^{-6}) / (0.36 \times 10^{-3}) \\
 &= 13324 \times 10^{-12 -6 +3} = 1.33 \times 10^{-11} \text{ F} \\
 Q &= CV = 1.20 \times 10^{-10} \text{ C}
 \end{aligned}$$

17) If the plates are pulled slightly further apart (increasing d) the magnitude of the *electric field* between the plates


- a. decreases.
- b. remains the same.
- c. increases.

$E = V/d$, V is constant, and d is increased, so E must go down.
In this case Q decreases, and $Q/\epsilon_0 A = E$ decreases.

18) If a dielectric of dielectric strength κ is placed between the plates, how will the charge on the capacitor change?

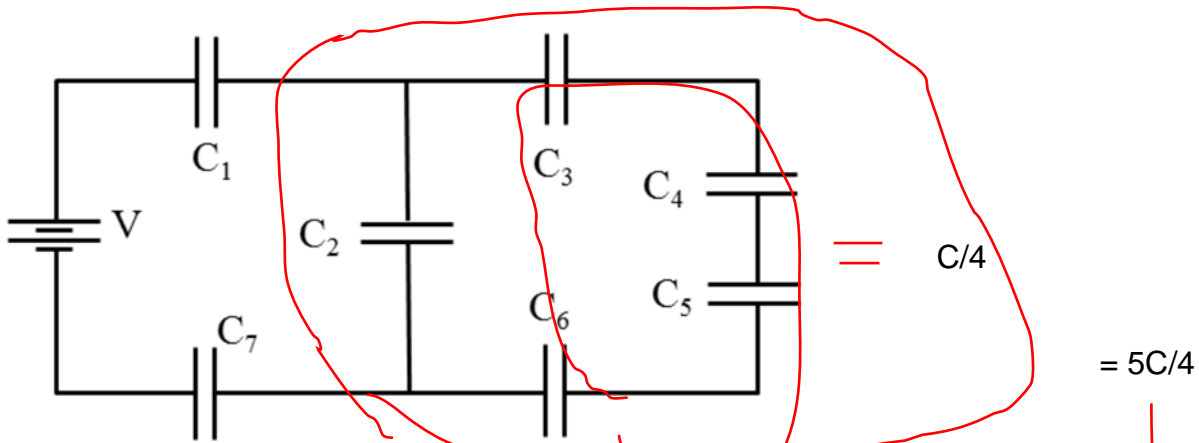- a. decrease by a factor of κ .
- b. Stay the same.
- c. Increase by a factor of κ .

The next four questions pertain to the situation described below.



Seven identical capacitors with capacitance $C = 8.5 \text{ nF}$ are connected to a 12 Volt battery as shown in the figure above.

19) Capacitors C_3 and C_6 are connected

- a. in parallel.
- b. in series.
- c. neither in series nor in parallel.

20) Compare the magnitude of the voltage across capacitor C_1 with the magnitude of the voltage across capacitor C_7

- a. $V_1 = V_7$
- b. $V_1 > V_7$
- c. $V_1 < V_7$

21) What is the equivalent capacitance of the network of seven capacitors?


- a. $C_{eq} = 9.92 \text{ nF}$
 - b. $C_{eq} = 9.07 \text{ nF}$
 - c. $C_{eq} = 23.8 \text{ nF}$
 - d. $C_{eq} = 3.04 \text{ nF}$
 - e. $C_{eq} = 1.21 \text{ nF}$
- $1/(2/C + 4/5C) = 0.357C = 3.0357 \text{ nF}$

22) What is the voltage across capacitor C_2 ?

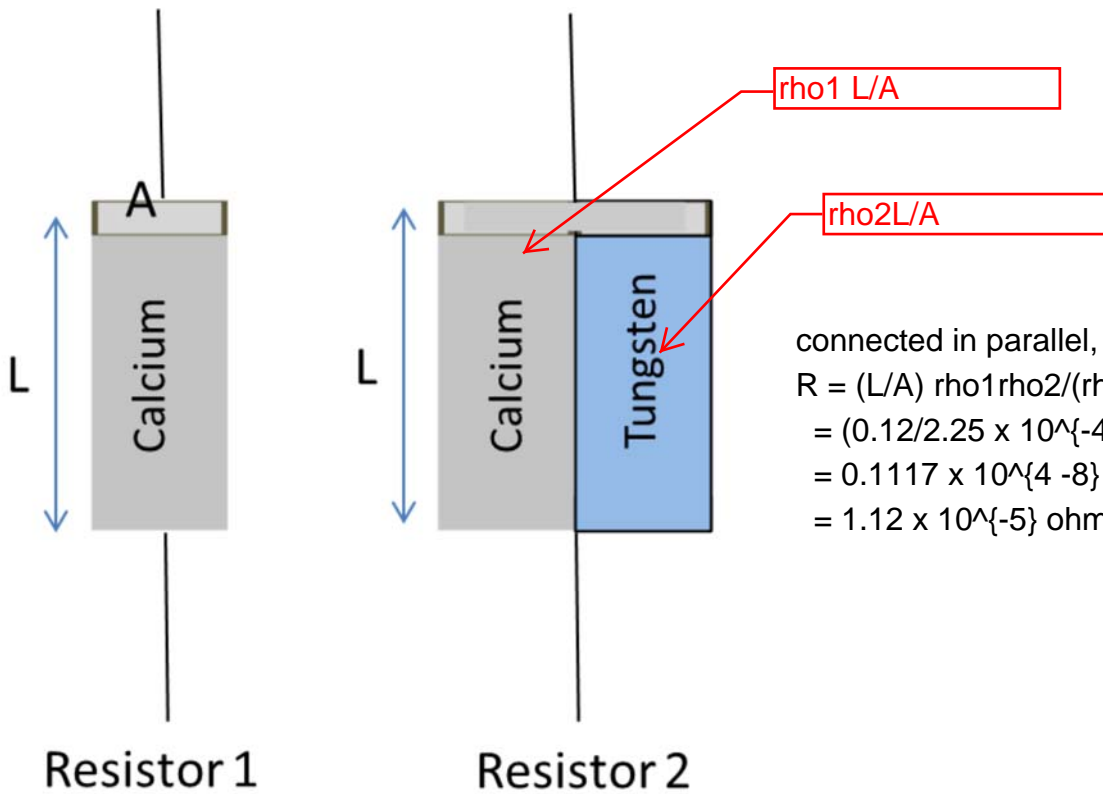- a. $V_2 = 3.4 \text{ Volts}$
- b. $V_2 = 4 \text{ Volts}$
- c. $V_2 = 0.85 \text{ Volts}$

Charges on the plates must be identical for C_1 , C_7 and the effective capacitor $C/4$.
 $V_1 C = V_7 C = V_2 (5C/4)$
 $V_1 + V_2 + V_7 = 12 \rightarrow (14/4) V_2 = 12$
 $V_2 = 3.4 \text{ V}$

The next two questions pertain to the situation described below.



connected in parallel, so

$$R = \frac{L}{A} \frac{\rho_1 \rho_2}{\rho_1 + \rho_2}$$

$$= \frac{0.12}{2.25 \times 10^{-4}} \frac{(5.6 \times 3.35) 10^{-8}}{8.96}$$

$$= 0.1117 \times 10^{-4}$$

$$= 1.12 \times 10^{-5} \text{ ohm.}$$

A student decides to build some resistors using rectangular blocks of calcium ($\rho = 3.36 \times 10^{-8} \Omega \text{ m}$) and tungsten ($\rho = 5.6 \times 10^{-8} \Omega \text{ m}$). The dimensions of the blocks are identical with a length $L = 0.12 \text{ m}$, and cross section $A = 2.25 \times 10^{-4} \text{ m}^2$. Resistor 1 is created from a single block of calcium. Resistor 2 is created by attaching a block of calcium to a block of tungsten as shown in the figure above.

23) Compare the resistance of the two resistors.

If you have more paths, R is smaller.

- a. $R_1 = R_2$
- b. $R_1 > R_2$
- c. $R_1 < R_2$

24) What is the resistance of resistor 2?

- a. $R_2 = 1.12 \times 10^{-5} \Omega$
- b. $R_2 = 4.78 \times 10^{-5} \Omega$
- c. $R_2 = 2.39 \times 10^{-5} \Omega$

Mechanics:

$$x = x_0 + v_0 t + \frac{1}{2} a t^2$$

$$v = v_0 + a t$$

$$F = m a$$

$$a_c = \frac{v^2}{r}$$

$$E_{tot} = K.E. + P.E.$$

$$K.E. = \frac{1}{2} m v^2 = \frac{p^2}{2m}$$

$$p = m v$$

$$W_F = F d \cos \theta$$

Electrostatics:

$$F_{12} = \frac{k q_1 q_2}{r^2}$$

$$E \equiv \frac{F}{q_0}$$

$$V \equiv \frac{U}{q_0}$$

$$\text{Point charge: } E = \frac{k q}{r^2}, \quad V = \frac{k q}{r}$$

$$U_{12} = \frac{k q_1 q_2}{r}$$

$$W_E = -\Delta U = -W_{you}$$

Capacitance:

$$C \equiv \frac{Q}{V}$$

$$\text{Parallel plate capacitor: } C = \frac{\kappa \epsilon_0 A}{d}, \quad V = E d$$

$$U_C = \frac{1}{2} Q V = \frac{1}{2} C V^2 = \frac{1}{2} \frac{Q^2}{C}$$

$$C_P = C_1 + C_2 + \dots$$

$$\frac{1}{C_S} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$

Resistance:

$$R \equiv \frac{V}{I}$$

$$I = \frac{\Delta q}{\Delta t}$$

$$\text{Physical resistance: } R = \rho \frac{L}{A}$$

$$P = I V = I^2 R = \frac{V^2}{R}$$

$$R_S = R_1 + R_2 + \dots$$

$$\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

Circuits:

$$\sum \Delta V = 0$$

$$\sum I_{in} = \sum I_{out}$$

$$q(t) = q_\infty (1 - e^{-t/\tau})$$

$$q(t) = q_0 e^{-t/\tau}$$

$$I(t) = I_0 e^{-t/\tau}$$

$$\tau = RC$$

Magnetism:

$$F = q v B \sin \theta$$

$$r = \frac{m v}{q B}$$

$$F = I L B \sin \theta$$

$$\tau = N I A B \sin \phi$$

$$B_{wire} = \frac{\mu_0 I}{2 \pi r}$$

$$B_{sol} = \mu_0 n I$$

Induction and inductance:

$$\varepsilon = -N \frac{\Delta \Phi}{\Delta t}$$

$$\Phi = B A \cos \phi$$

$$\varepsilon_{bar} = B L v$$

$$\varepsilon_{gen} = \varepsilon_{max} \sin \omega t = \omega N A B \sin \omega t$$

$$\omega = 2 \pi f$$

$$L \equiv \frac{N \Phi}{I}$$

$$\varepsilon = -L \frac{\Delta I}{\Delta t}$$

$$\text{Solenoid inductor: } L = \mu_0 n^2 A \ell$$

$$U_L = \frac{1}{2} L I^2$$

AC circuits and transformers:

$$V_{rms} = \frac{V_{max}}{\sqrt{2}} \quad I_{rms} = \frac{I_{max}}{\sqrt{2}} \quad \frac{V_p}{V_s} = \frac{I_s}{I_p} = \frac{N_p}{N_s}$$

$$V_R(t) = V_{R,max} \sin(\omega t) = I_{max} R \sin(\omega t) \quad \omega = 2\pi f$$

$$V_C(t) = V_{C,max} \sin(\omega t - \pi/2) = I_{max} X_C \sin(\omega t - \pi/2) \quad X_C \equiv \frac{1}{\omega C}$$

$$V_L(t) = V_{L,max} \sin(\omega t + \pi/2) = I_{max} X_L \sin(\omega t + \pi/2) \quad X_L \equiv \omega L$$

$$V_{gen}(t) = V_{gen,max} \sin(\omega t + \phi) = I_{max} Z \sin(\omega t + \phi) \quad Z \equiv \sqrt{R^2 + (X_L - X_C)^2} \quad \tan \phi = \frac{X_L - X_C}{R}$$

$$\bar{P} = I_{rms} V_{R,rms} = I_{rms} V_{gen,rms} \cos \phi \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Electromagnetic waves:

$$\lambda = \frac{c}{f} \quad E = cB$$

$$u_E = \frac{1}{2} \epsilon_0 E^2 \quad u_B = \frac{1}{2\mu_0} B^2 \quad \bar{u} = \frac{1}{2} \epsilon_0 E_{rms}^2 + \frac{1}{2\mu_0} B_{rms}^2 = \epsilon_0 E_{rms}^2 = \frac{B_{rms}^2}{\mu_0} \quad S = I = \bar{u}c$$

$$f' = f \left(1 \pm \frac{u}{c} \right) \quad I = I_0 \cos^2 \theta$$

Reflection and refraction:

$$\theta_r = \theta_i \quad \frac{1}{d_o} + \frac{1}{d_i} = \frac{1}{f} \quad f = \pm \frac{R}{2} \quad m = \frac{h_i}{h_o} = -\frac{d_i}{d_o}$$

$$n_1 \sin \theta_1 = n_2 \sin \theta_2 \quad v = \frac{c}{n} \quad \sin \theta_c = \frac{n_2}{n_1} \quad M = \frac{\theta'}{\theta} \approx \frac{d_{near}}{f}$$

Interference and diffraction:

Double slit interference: $d \sin \theta = m\lambda$ $d \sin \theta = (m + \frac{1}{2})\lambda$ $m = 0, \pm 1, \pm 2, \dots$

Single-slit diffraction: $w \sin \theta = m\lambda$ $m = \pm 1, \pm 2, \dots$

Circular aperture: $D \sin \theta \approx 1.22\lambda$

Thin film: $\delta_1 = (0 \text{ or } \frac{1}{2})\lambda$ $\delta_2 = (0 \text{ or } \frac{1}{2})\lambda + 2t \frac{n_{film}}{\lambda_0}$ $|\delta_2 - \delta_1| = (m \text{ or } m + \frac{1}{2})\lambda$ $m = 0, 1, 2, \dots$

Quantum mechanics:

$$E = hf = \frac{hc}{\lambda} \quad \lambda = \frac{h}{p}$$

Blackbody radiation: $\lambda_{max} T = 2.898 \times 10^{-3} \text{ m} \cdot \text{K}$ Photoelectric effect: $K.E. = hf - W_0$

$$\Delta p_x \Delta x \geq \frac{\hbar}{2} \quad \hbar \equiv \frac{h}{2\pi}$$

Bohr atom: $2\pi r_n = n\lambda$ $n = 1, 2, 3, \dots$ $L_n = m v_n r_n = n\hbar$

$$r_n = \left(\frac{\hbar^2}{mke^2} \right) \frac{n^2}{Z} \approx (5.29 \times 10^{-11} \text{ m}) \frac{n^2}{Z}$$

$$\frac{1}{\lambda} \approx (1.097 \times 10^7 \text{ m}^{-1}) Z^2 \left(\frac{1}{n_f^2} - \frac{1}{n_i^2} \right)$$

Quantum atom: $L = \sqrt{\ell(\ell+1)}\hbar$

$$E_n = - \left(\frac{mk^2e^4}{2\hbar^2} \right) \frac{Z^2}{n^2} \approx -(13.6 \text{ eV}) \frac{Z^2}{n^2}$$

$$L_z = m_\ell \hbar$$

Nuclear physics and radioactive decay:

$$A = Z + N$$

$$r \approx (1.2 \times 10^{-15} \text{ m}) A^{1/3}$$

$$E_0 = mc^2$$

$$\frac{\Delta N}{\Delta t} = -\lambda N$$

$$N(t) = N_0 e^{-\lambda t} = N_0 2^{-t/T_{1/2}}$$

$$T_{1/2} \equiv \frac{\ln 2}{\lambda} \approx \frac{0.693}{\lambda}$$

Special relativity:

$$\Delta t = \gamma \Delta t_0$$

$$L = \frac{L_0}{\gamma}$$

$$\gamma \equiv \frac{1}{\sqrt{1 - \frac{v^2}{c^2}}}$$

Constants and unit conversions:

$$g = 9.8 \text{ m/s}^2$$

$$e = 1.60 \times 10^{-19} \text{ C}$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2 / \text{Nm}^2$$

$$k \equiv \frac{1}{4\pi\epsilon_0} = 8.99 \times 10^9 \text{ Nm}^2 / \text{C}^2$$

$$\mu_0 = 4\pi \times 10^{-7} \text{ T} \cdot \text{m} / \text{A}$$

$$c = \frac{1}{\sqrt{\epsilon_0 \mu_0}} = 3 \times 10^8 \text{ m/s}$$

$$h = 6.626 \times 10^{-34} \text{ J} \cdot \text{s}$$

$$hc = 1240 \text{ nm} \cdot \text{eV}$$

$$1 \text{ eV} = 1.60 \times 10^{-19} \text{ J}$$

$$m_{\text{proton}} = 1.67 \times 10^{-27} \text{ kg} = 938 \text{ MeV}$$

$$m_{\text{electron}} = 9.11 \times 10^{-31} \text{ kg} = 511 \text{ keV}$$

SI Prefixes		
Power	Prefix	Symbol
10^9	giga	G
10^6	mega	M
10^3	kilo	k
10^0	—	—
10^{-3}	milli	m
10^{-6}	micro	μ
10^{-9}	nano	n
10^{-12}	pico	p

Physics 102 Exam 1 --
Spring 2014

1. d
2. a
3. c
4. c
5. e
6. c
7. b
8. c
9. b
10. c
11. b
12. b
13. a
14. d
15. a
16. cd
17. a
18. c
19. b
20. a
21. d
22. a
23. b
24. a