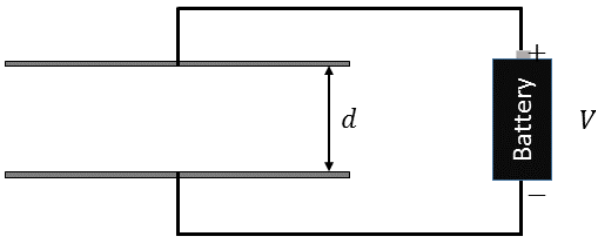





The next two questions pertain to the situation described below.

Consider a parallel plate capacitor with separation d :




It is connected to a battery with constant emf V .

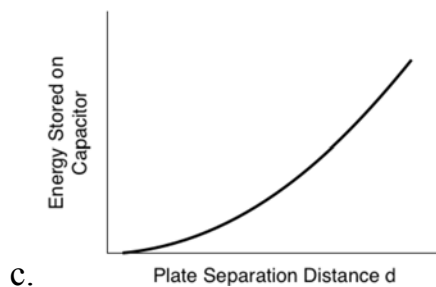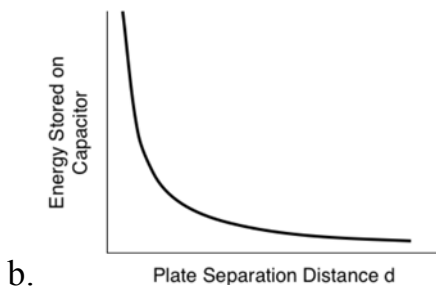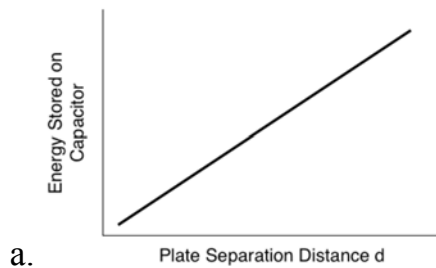1) Which diagram best describes the energy stored in the capacitor as a function of the separation distance d while the capacitor is connected to the battery?



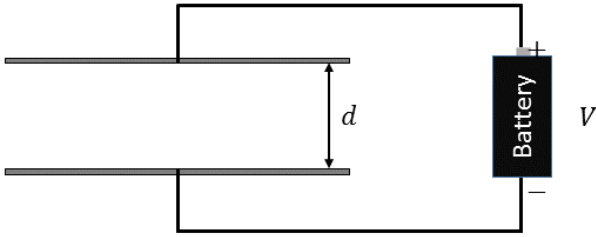2) The battery provides an emf $V = 9$ V. Once the capacitor is fully charged the battery is disconnected. What energy is stored in the capacitor?




The separation distance is $d = 3$ mm and the plate area is $A = 5500$ mm². The capacitor gap is filled with vacuum ($\kappa = 1$).

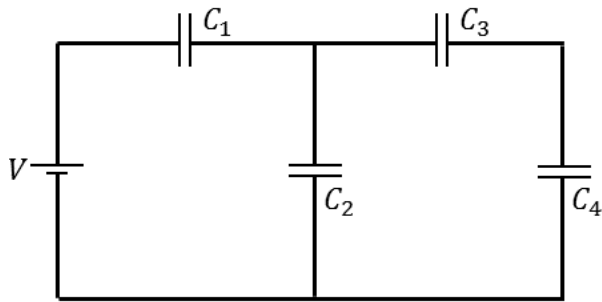- a. $E = 0.07$ nJ
- b. $E = 2.64$ nJ
- c. $E = 0.66$ nJ
- d. $E = 0$ nJ
- e. $E = 1.32$ nJ

The next two questions pertain to the situation described below.

Consider the following capacitor network:






All capacitors in this network are the same and have capacitance $C = 6 \mu\text{F}$. The network is connected to a battery that provides a potential difference $V = 9 \text{ V}$.


- 3) The equivalent capacitance of the branch containing capacitors C_3 and C_4 is
- a. $2C$
 - b. $C/2$
 - c. C
- 4) What is the charge on capacitor C_2 after the network has been connected to the battery for a long time?
- a. $Q_2 = 21.6 \mu\text{C}$
 - b. $Q_2 = 135 \mu\text{C}$
 - c. $Q_2 = 18 \mu\text{C}$
 - d. $Q_2 = 13.5 \mu\text{C}$
 - e. $Q_2 = 72 \mu\text{C}$

The next two questions pertain to the situation described below.

Consider the three resistors shown. They each have *known dimensions*, listed in the table, but *unknown resistivities*.

You attach each resistor to a battery of known voltage, V , and measure the power dissipated by the resistors. The measurements are recorded in the table:

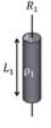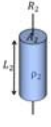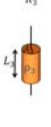
Resistor	Length (mm)	Area (mm ²)	Power Dissipated (W)
 R_1	$L_1 = 40$	$A_1 = 2$	$P_1 = 200$
 R_2	$L_2 = 40$	$A_2 = 8$	$P_2 = 400$
 R_3	$L_3 = 20$	$A_3 = 2$	$P_3 = 200$

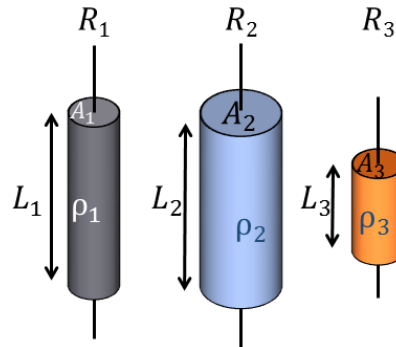

5) What conclusion can you draw about the *resistivities* of resistors R_2 and R_3 ?

- a. $\rho_2 = \rho_3$
- b. $\rho_2 < \rho_3$
- c. $\rho_2 > \rho_3$

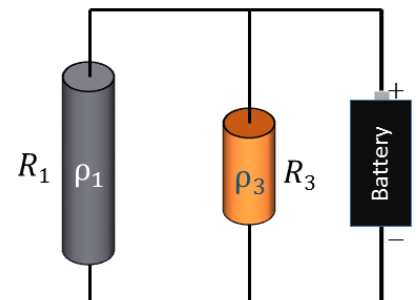
6) Resistors R_1 and R_3 are placed in parallel and attached to the battery (with voltage V). The total power dissipated by these resistors in parallel will be



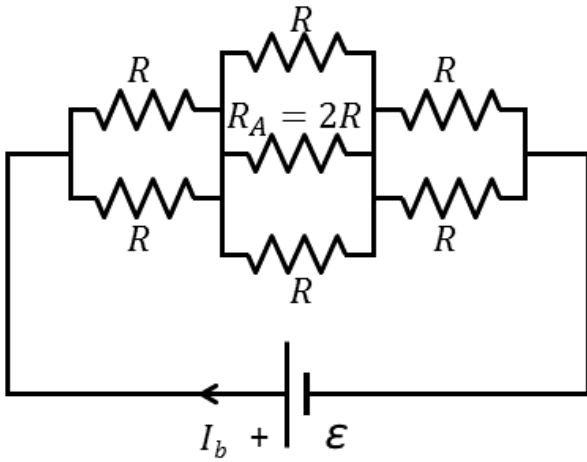- a. $P_1/2$
- b. $2P_1$
- c. P_1

The next two questions pertain to the situation described below.

Consider the following network of resistors. The network is connected to a battery, with emf ε , through which a current I_b passes.



All resistors *except* R_A have resistance R . Resistor $R_A = 2R$.

7) Calculate the equivalent resistance, R_{eq} , of the network.


- a. $R_{eq} = R/3$
- b. $R_{eq} = R/2$
- c. $R_{eq} = 7R/5$
- d. $R_{eq} = 2R/5$
- e. $R_{eq} = R$

8) Calculate the current I_A through resistor R_A in terms of the battery current I_b .

- a. $I_A = I_b/5$
- b. $I_A = I_b/3$
- c. $I_A = 2I_b$
- d. $I_A = I_b/2$
- e. $I_A = I_b$

The next three questions pertain to the situation described below.

Consider this circuit.

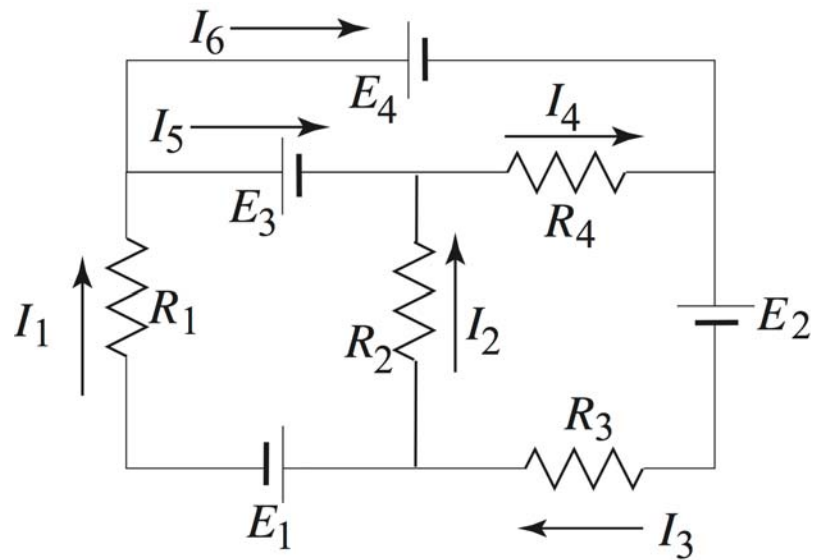

9) Choose the correct relation among the branch currents from the following five equalities.

- a. $I_4 - I_2 + I_1 = 0$
- b. $I_1 - I_5 + I_6 = 0$
- c. $I_2 - I_1 - I_3 = 0$
- d. $I_5 - I_2 - I_4 = 0$
- e. $I_3 - I_6 - I_4 = 0$

10) This network has several closed loops.

From among the following 5 equalities, which **does not** describe a loop in this network?

- a. $R_1 I_1 + E_1 - R_2 I_2 + E_3 = 0$
- b. $-R_1 I_1 - E_3 - R_4 I_4 - E_2 - R_3 I_3 - E_1 = 0$
- c. $E_4 - E_3 - I_4 R_4 = 0$
- d. $E_4 - E_3 + R_2 I_2 + R_3 I_3 + E_2 = 0$
- e. $-R_2 I_2 - R_4 I_4 - E_2 + R_3 I_3 = 0$


11) Suppose:

$$R_1 = R_2 = R_3 = R_4 = 20 \Omega.$$

$$E_1 = E_2 = E_3 = 25 \text{ V.}$$

$$E_4 = 55 \text{ V.}$$


What is the current I_6 ?

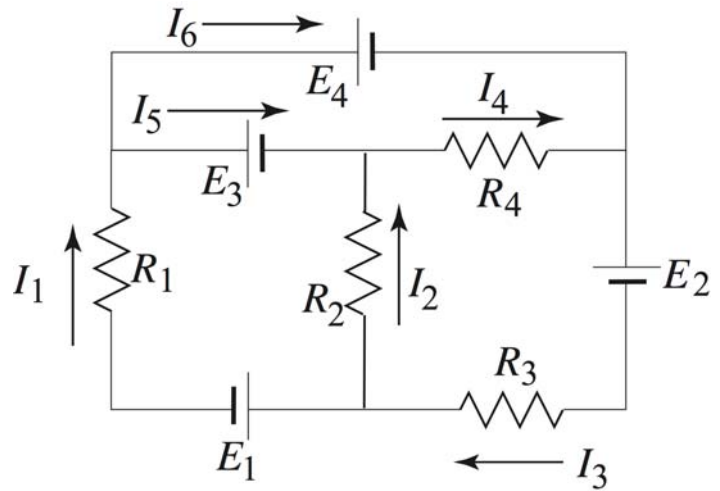

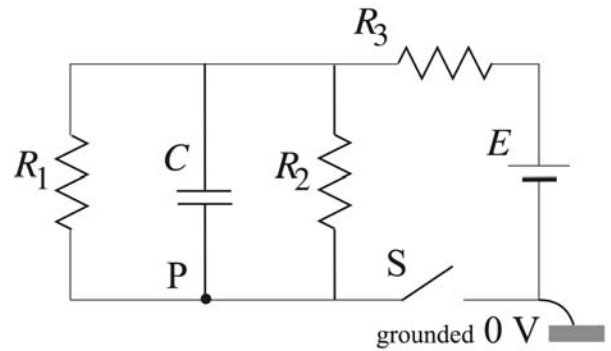- a. $I_6 = 1.5 \text{ A}$
- b. $I_6 = -1.5 \text{ A}$
- c. $I_6 = 4 \text{ A}$

The next four questions pertain to the situation described below.


In the following circuit $R_1 = R_2 = R_3 = 20 \Omega$,
 $C = 0.35 \text{ F}$, and $E = 90 \text{ V}$. Initially the switch S is open for a long time.



12) What is the voltage at point P? The switch, S, is open.

- a. $V_P = 0 \text{ V}$
- b. $V_P = 90 \text{ V}$
- c. $V_P = 30 \text{ V}$
- d. $V_P = 45 \text{ V}$
- e. $V_P = 15 \text{ V}$

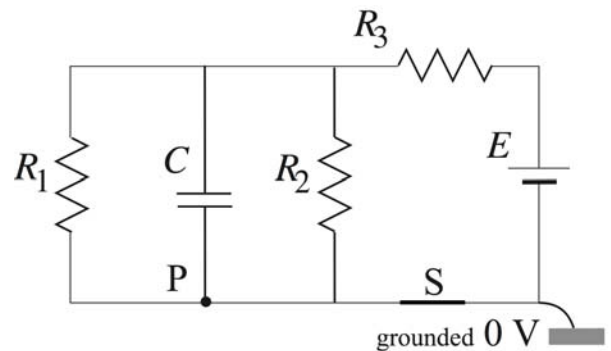13) What is the current I_2 through R_2 and the current I_3 through R_3 immediately after the switch, S, is closed? Choose the right combination.




- a. $I_2 = 0 \text{ A}, I_3 = 4.5 \text{ A}$.
- b. $I_2 = 1.5 \text{ A}, I_3 = 4.5 \text{ A}$.
- c. $I_2 = 0 \text{ A}, I_3 = 2.25 \text{ A}$.
- d. $I_2 = 1.5 \text{ A}, I_3 = 2.25 \text{ A}$.
- e. $I_2 = 4.5 \text{ A}, I_3 = 4.5 \text{ A}$.

14) What is the charge stored in capacitor C long after switch, S , is closed for a long time?

- a. $Q = 31.5 \text{ C}$
- b. $Q = 0 \text{ C}$
- c. $Q = 15.75 \text{ C}$
- d. $Q = 10.5 \text{ C}$
- e. $Q = 21 \text{ C}$

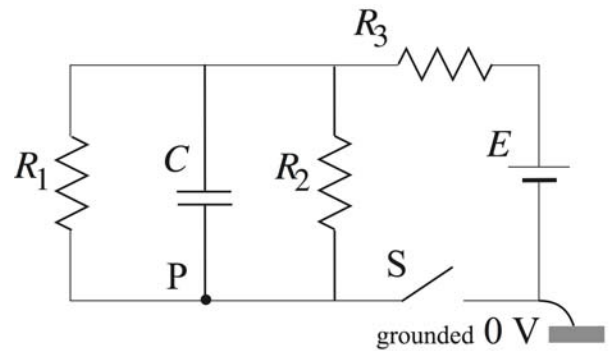15) After a long time since switch, S , is closed, the switch is opened again. How long does it take for the stored charge to be halved?




- a. $t = 3.82 \text{ s}$
- b. $t = 2.43 \text{ s}$
- c. $t = 2.14 \text{ s}$
- d. $t = 5.42 \text{ s}$
- e. $t = 4.37 \text{ s}$

The next two questions pertain to the situation described below.

Two charges of equal magnitude and opposite sign are positioned in a uniform magnetic field (gray lines).

The charges travel in the plane of the page, at velocities v_1 and v_2 with $|v_1| = |v_2|$ at the angles shown

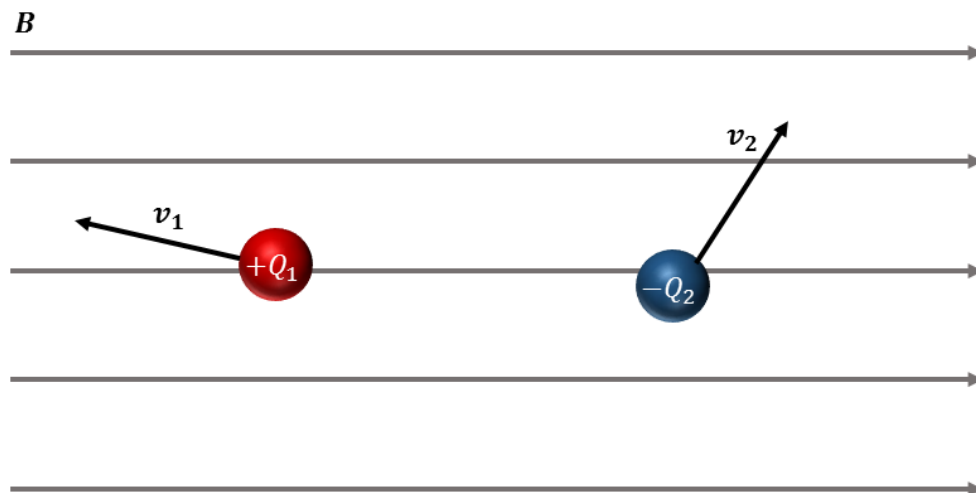

16) What charge experiences the largest force due to the magnetic field?


- a. Charge 1 ($+Q_1$)
- b. Charge 2 ($-Q_2$)
- c. They experience the same force.

17) What is the direction of the force on charge 2?

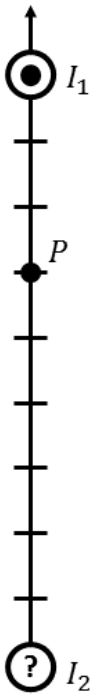- a. To the right
- b. Out of the page
- c. Into the page

The next two questions pertain to the situation described below.

Two wires are shown in the diagram. Wire 1 carries current I_1 out of the page. Wire 2 carries current I_2 of unknown magnitude and direction.



The magnetic field at point P is zero.

18) What direction is the current traveling in wire two?


- a. into page
- b. out of page
- c. no current

19) What is the magnitude of I_2 ?

- a. $I_2 = 2I_1$
- b. $I_2 = 4I_1$
- c. $I_2 = I_1/2$

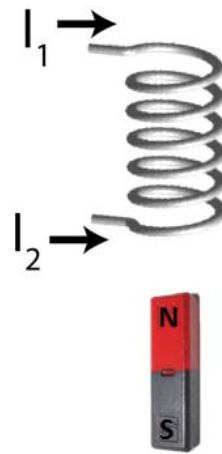20) The diagram shows a permanent magnet with its north pole oriented up. Above the magnet is a solenoid.


In what direction should current flow through the solenoid so that the solenoid **repels the magnet**?






- a. I_2
- b. No current is necessary.
- c. I_1

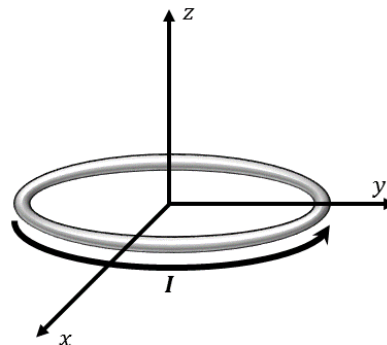21) A loop of wire carries a current I and sits in the xy -plane as shown in the figure.


Which figure best describes the **direction** of the magnetic dipole moment produced by this current loop?



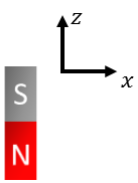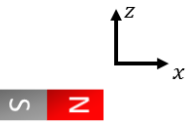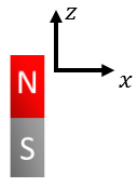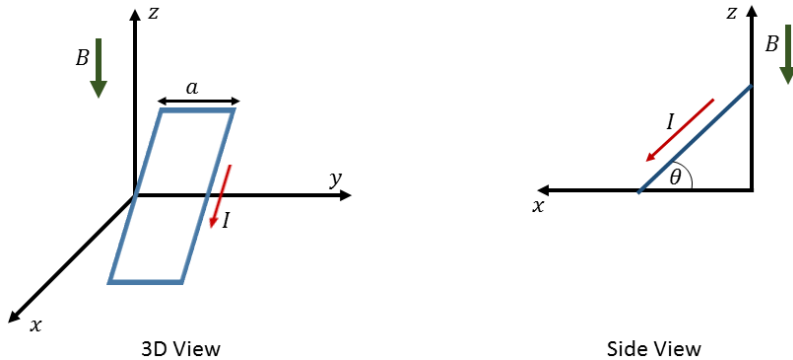- a. 
- b. 
- c. 

The next three questions pertain to the situation described below.

A rectangular loop (blue) carries a current $I = 1$ A. The current flows in the direction shown by the red arrow. The area of the loop is 0.1 m^2 . The loop is at an angle $\theta = 40^\circ$ with the xy -plane (side view). A uniform magnetic field $B = 1$ T is in the $-z$ direction. One segment of the loop is labeled a .




22) What is the direction of the force on segment a of the loop due to the magnetic field?

- a. $+y$
- b. $+x$
- c. $-x$
- d. $-y$
- e. $+z$

23) What is the magnitude of the torque on the loop?

- a. $|\tau| = 0.129 \text{ N} \cdot \text{m}$
- b. $|\tau| = 0.1 \text{ N} \cdot \text{m}$
- c. $|\tau| = 0.064 \text{ N} \cdot \text{m}$

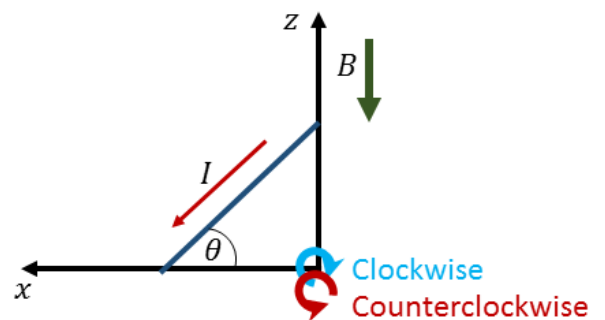24) In the **Side View** representation of the loop what direction does the loop rotate?



- a. clockwise
- b. counterclockwise
- c. does not rotate