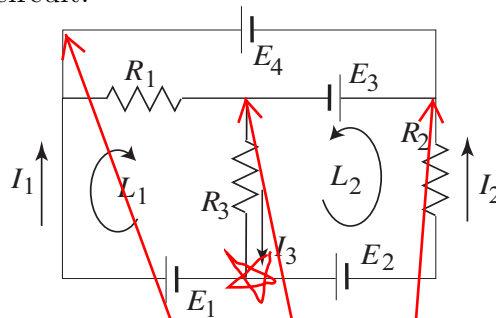


Name: _____ Section: _____ Score: _____/20

1. Consider the following circuit.



(1) What is the relation among I_1 , I_2 and I_3 [3]?

Kirchhoff junction rule

Consider the red star junction: I_3 comes in, but I_1 and I_2 go out. Hence $I_3 - I_1 - I_2 = 0$.

(2) Write down the loop equation for loop L_2 [3].

current direction going down

I_2 goes down.

E_3 goes down

I_3 goes down

E_2 goes down.

Hence, $-I_2R_2 - E_3 - I_3R_3 - E_2 = 0$

Let us assume this is 0V. Then

5 V here

10 V here

(3) Find the current through R_1 . Assume all resistors are 2Ω and all the batteries supply 5 V. [4].


Ohm's law

Thus, the voltage across R_1 is 10 V.

Therefore, $I = 10/R_1 = 10/2 = 5 \text{ A}$.

Try to draw an effective circuit.

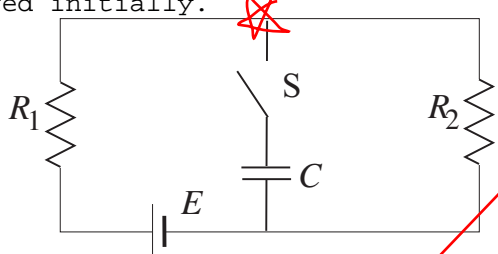2. The voltage $E = 20\text{ V}$, $R_1 = R_2 = 1\text{ k}\Omega$ and the capacitance $C = 5\text{ }\mu\text{F}$. C is uncharged initially.



Principle:
The voltage across C cannot change immediately.

(1) Switch S has been open for a long time. What is the current through resistor R_1 ? [3]




series connection; Ohm's law

$$I = E / (R_1 + R_2) = 20 / 2000 = 0.01\text{ A.}$$

The middle branch has no current initially, so even if you remove it, nothing happens.

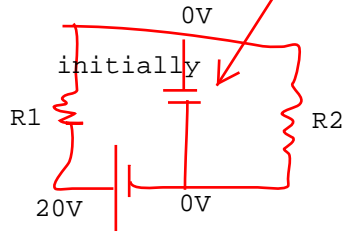(2) Now, at $t = 0$ switch S is closed. What are the current I_1 through R_1 and current I_2 through R_2 immediately after the switch is closed? [4]

Thus, the voltage across C is zero. Therefore, the voltage across R_2 is 0, so $I_2 = 0$.
Across R_1 the voltage is $E = 20\text{ V}$. $I_1 = E / R_1 = 20 / 1000 = 0.02\text{ A}$.



(3) After a long time what is the charge stored in the capacitor C ? [3]

After a long time, C is filled up.
No current through it

The effective circuit is just as (1). Thus, the voltage at the star junction is $E/2 = 10\text{ V}$. Therefore, the voltage across C is 10 V .

$$Q = CV = 5 \times 10^{-6} \times 10 = 50\text{ microC.}$$

