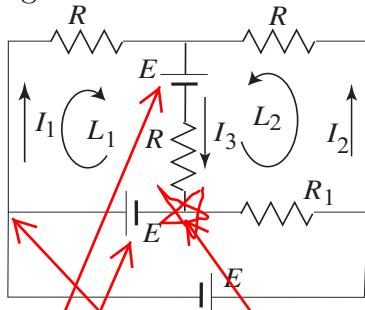


Name: _____ Section: _____ Score: _____ /20

1. Consider the following circuit.



- (1) What is the relation among I_1 , I_2 and I_3 [3]?

Kirchhoff junction rule

Consider the red star junction: I_3 comes in, but I_1 and I_2 go out. Hence $I_3 - I_1 - I_2 = 0$.

- (2) Write down the loop equation for loop L_1 [3].

current direction going down

I_1 goes down.

E goes down

I_3 goes down

E goes up.

Hence, $-I_1R -E - I_3R + E = (I_1 + I_3)R$.

Assume this is 0 V

4 V here

8 V here.


- (3) Find the current through R_1 . Assume all resistors are $6\ \Omega$ and all the batteries supply 4 V. [4].

Ohm's law

Thus, the voltage across R_1 is 8 V.

Therefore, $I = 8/R_1 = 8/6 = 1.33\ A$.

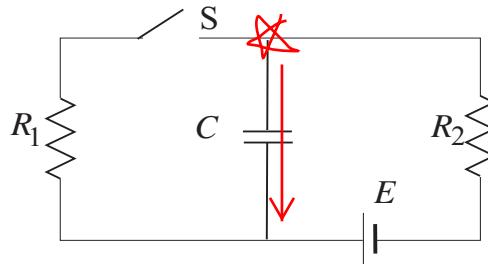2. The voltage $E = 20 \text{ V}$, $R_1 = R_2 = 1 \text{ k}\Omega$ and the capacitance $C = 3 \mu\text{F}$. Initially, the switch S is open for a long time.




Principle:
The voltage across C cannot change immediately.

- (1) What is the charge stored in capacitor C? [3]

After a long time there is no current across C.

Try to draw an effective circuit.

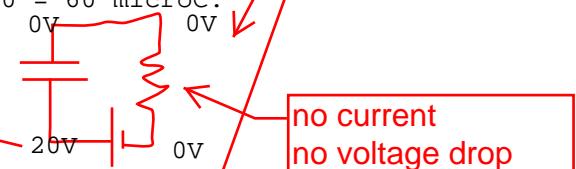Thus, there is no current, so no voltage drop across R_2 . Thus, the voltage across C is E. Hence. $Q = CV = 3 \times 10^{-6} \times 20 = 60 \mu\text{C}$.




no current
no voltage drop

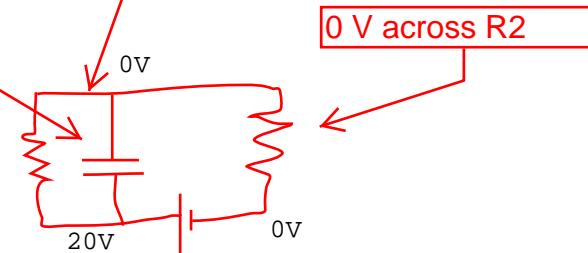- (2) Immediately after switch S is closed, what are the current I_1 through R_1 and the current I_2 through R_2 ? [4]

Thus, the voltage across C is 20 V with the red arrow as the direction ascending voltage.

There. there is no voltage across $R_2 \rightarrow I_2 = 0$.
20 V across $R_1 \rightarrow I_1 = 20/R_1 = 20/1000 = 0.02 \text{ A}$.



0 V across R_2

- (3) Long time after switch S is closed, what is the charge stored in capacitor C? [3]

C is full, and no current through it.

The voltage at the red star is $E/2$.

Thus 10 V across C $\rightarrow Q = CV = 3 \times 10^{-6} \times 10 = 30 \mu\text{C}$.

no current through C, so you can remove this to consider the circuit

